
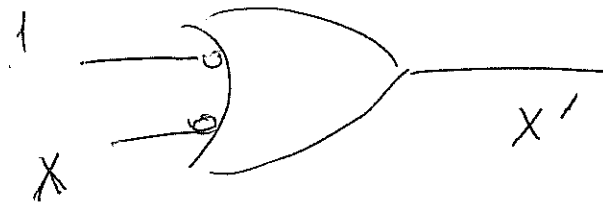


EECS 281, March 17, 2015

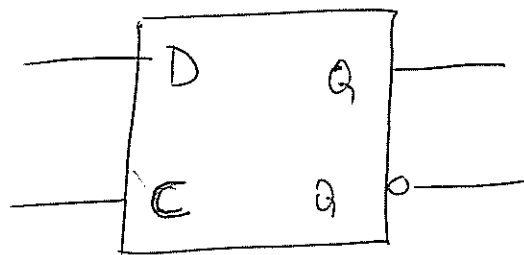

D - latch:



| C | D | Q | Q _N |
|---|---|--------|---------------------|
| 0 | X | last Q | last Q _N |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

D latch is used to store bits of information.

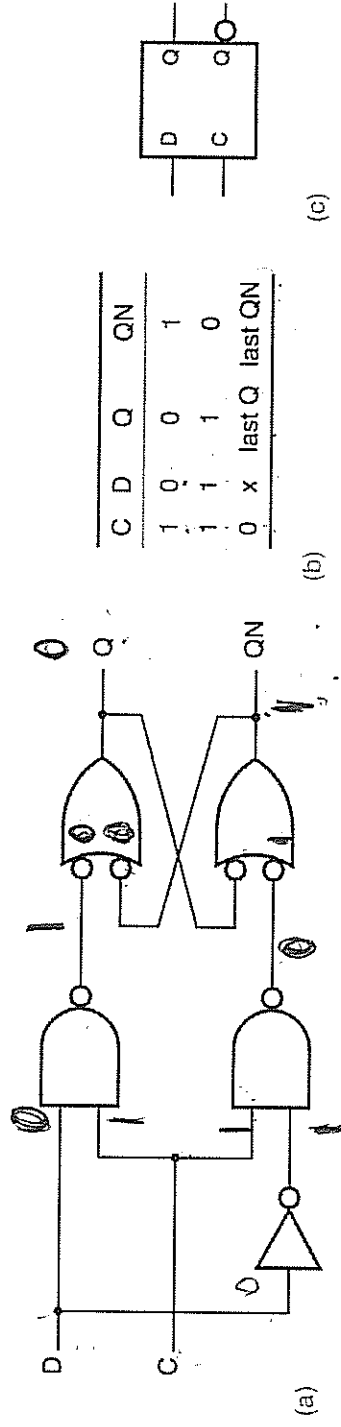


Figure 7-12

D latch: (a) circuit design using NAND gates; (b) function table; (c) logic symbol.

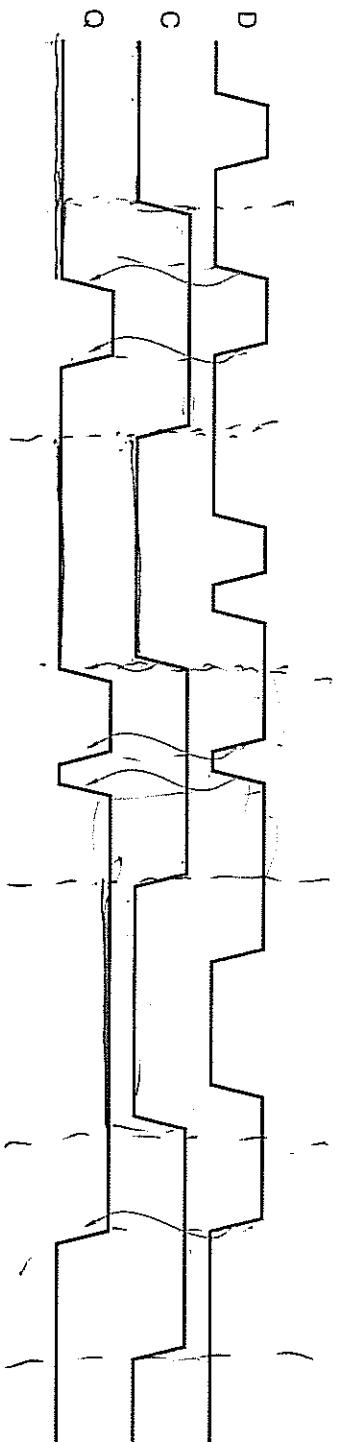


Figure 7-13

Functional behavior of a D latch for various inputs.

meta stability: still a problem.


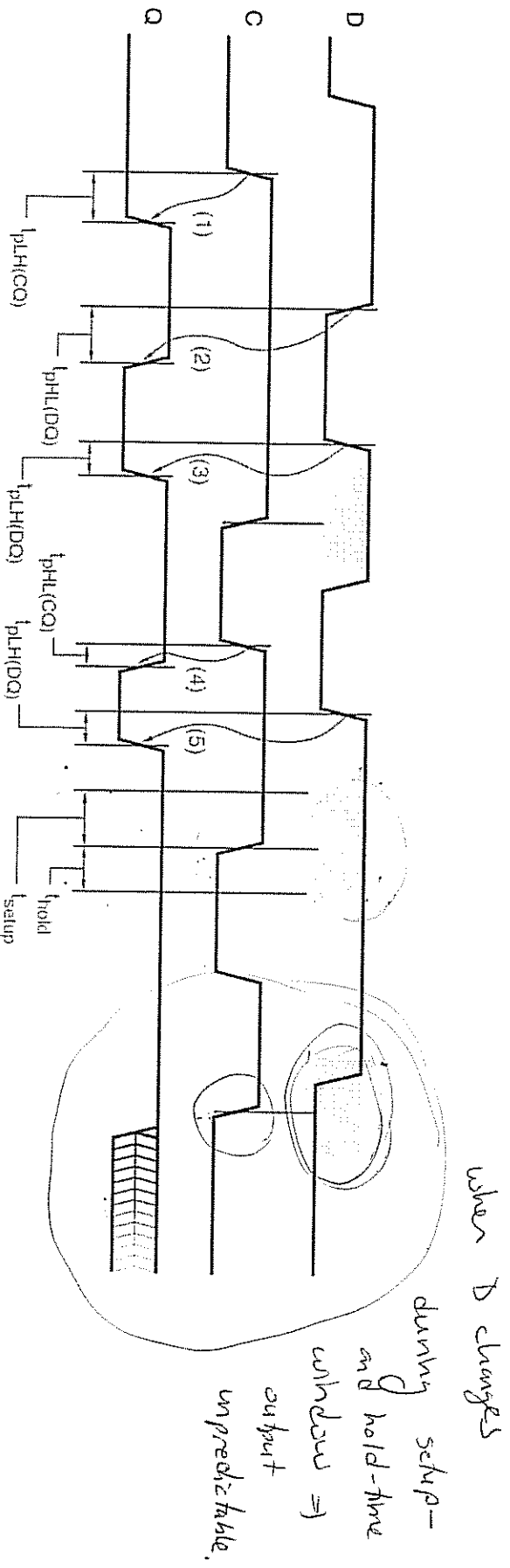



Figure 7-14

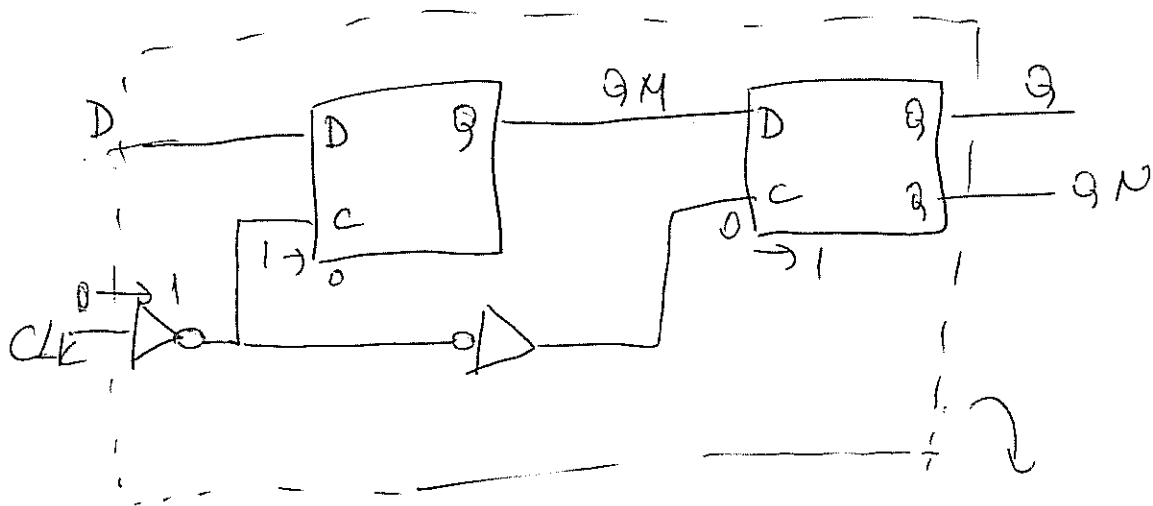

Timing parameters for a D latch.

Positive-Edge Triggered D Flip-Flop

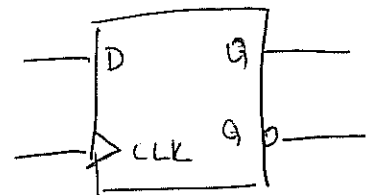

CLK = 0. \rightarrow 1



| D | CLK | Q | QN |
|---|---|--------|---------|
| X | 0 | last Q | last QN |
| X | 1 | last Q | last QN |
| 0 |  | 0 | 1 |
| 1 |  | 1 | 0 |

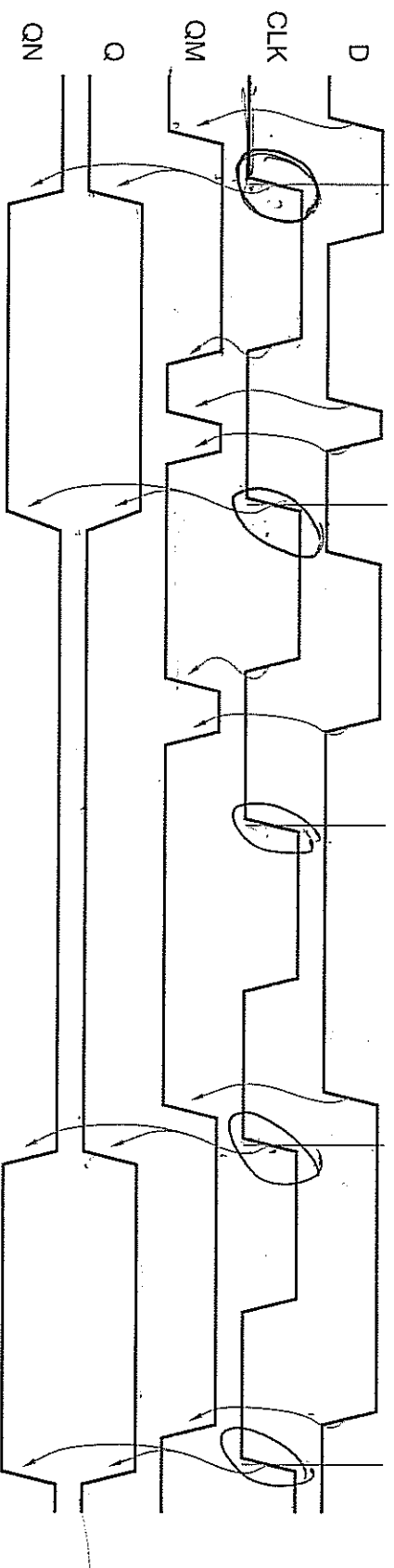


Figure 7-16

Functional behavior of a positive-edge-triggered D flip-flop.

2-input mux controls the value applied to flip-flop D input.

$EN = 1 \Rightarrow$ external D is input to internal D.

$EN = 0 \Rightarrow$ current Q is used as input to internal D


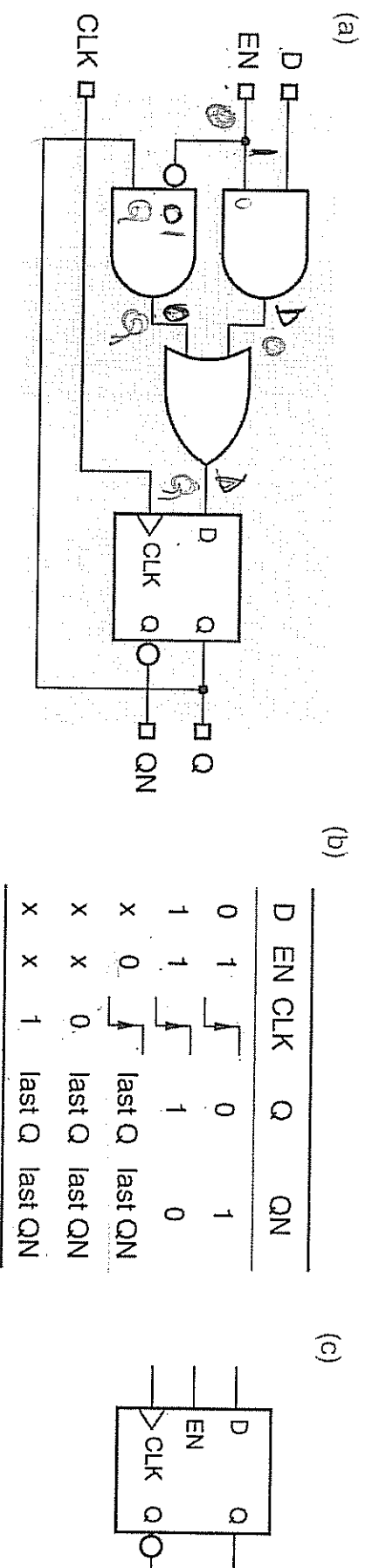


Figure 7-21

Positive-edge-triggered D flip-flop with enable: (a) circuit design; (b) function table; (c) logic symbol.

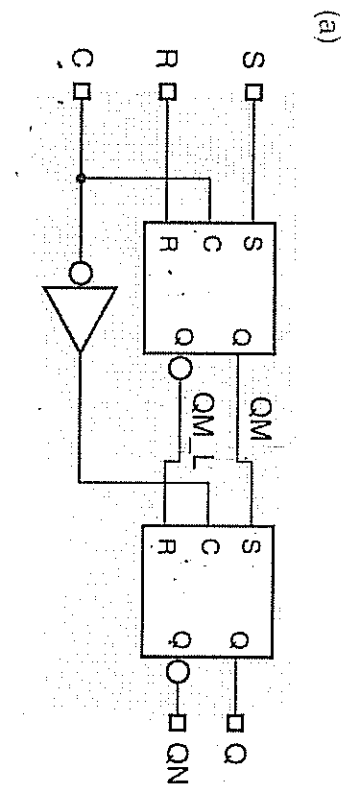S-R flip-flop: changes output only at falling edge of C.
 (negative-edge-triggered)
 output depends on input values not just at falling edge, but during entire interval when C=1.



(b)

| S | R | C | Q | QN |
|---|---|---|--------|---------|
| x | x | 0 | last Q | last QN |
| 0 | 0 | 1 | last Q | last QN |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | undef. | undef. |

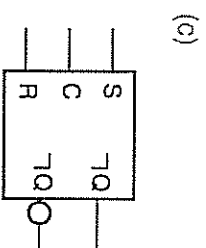


Figure 7-24
 Master/slave S-R flip-flop: (a) circuit using S-R latches; (b) function table; (c) logic symbol.

postponed output +
 indicators: output +
 does not change
 with C negated.

unpredictable: If both $S = R = 1$ at falling edge of C .


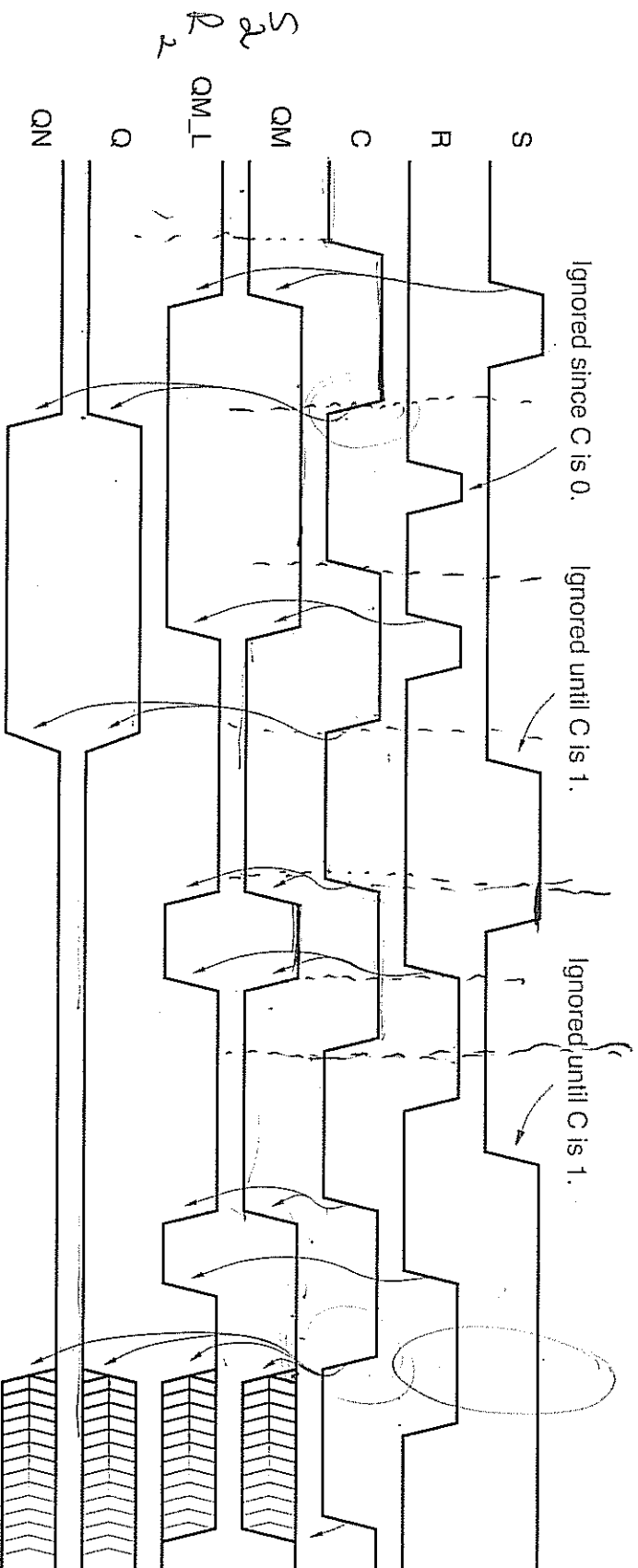


Figure 7-25

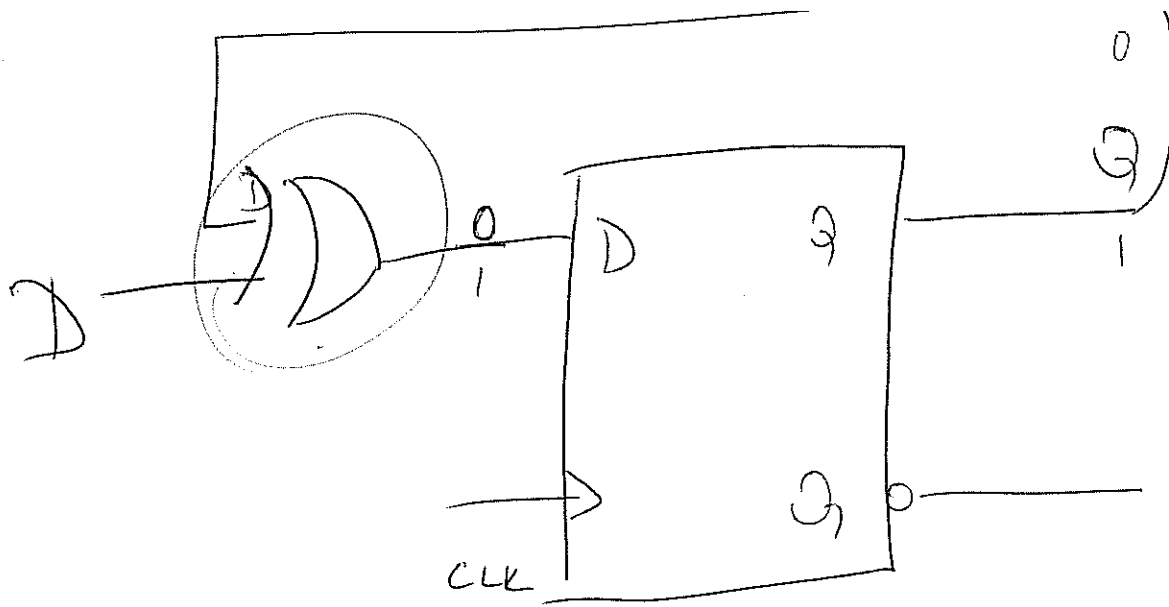Internal and functional behavior of a master/slave S-R flip-flop.



| | | | | | | |
|-----|---|---|---|---|---|---|
| D | 0 | 1 | 1 | 0 | 1 | 1 |
| Q | 0 | 0 | 1 | 0 | 0 | 1 |

| Q | D | Q^* |
|-----|-----|-------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |