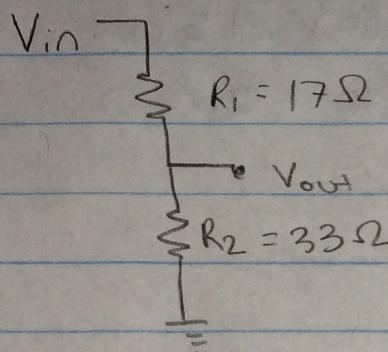


GSA #2

9/10/15



$$\textcircled{1} \quad V_{\text{out}} = \frac{R_2}{R_1 + R_2} (V_{\text{in}})$$

$$3.3 = \frac{R_2}{R_1 + R_2} (5)$$

$$3.3 = \frac{33}{17 + 33}$$

$$3.3 = \frac{33}{50}$$

$$R_2 = 33\Omega$$

$$R_1 + R_2 = 50$$

$$R_1 + 33 = 50$$

$$R_1 = 17\Omega$$

$$\textcircled{2} \quad \text{Approx: } \frac{17}{33} = \frac{R_1}{R_2}$$

$$R_1 = 220\Omega$$

$$R_2 = 430\Omega$$

$$V_{\text{out}} = \frac{R_2}{R_1 + R_2} (V_{\text{in}}) = \frac{430}{220 + 430} 5V = 3.3V$$

$$\textcircled{3} \quad R_{\text{tot}} = R_1 + R_2 = 220 + 430 = 650\Omega$$

$$V = IR \Rightarrow I = \frac{V}{R_{\text{tot}}} = \frac{5V}{650\Omega} = 0.0077A$$

$$P_{R_1} = I^2 R = 0.0077^2 \times 220\Omega$$
$$= 0.013W$$

$$P_{R_2} = I^2 R = 0.0077^2 \times 430\Omega$$
$$= 0.025W$$

#4

$$R_1 = 220 \Omega \quad R_2 = 430 \Omega$$

$$220 (.05) = 11 \Omega \quad 430 (.05) = 21.5 \Omega$$

$$R_1 = 220 \pm 11 \Omega \quad R_2 = 430 \pm 21.5 \Omega$$

$$V_{out} \underset{R_1 \text{ low}}{\overset{R_2 \text{ both}}{=}} 3.31 V$$

$$V_{out} \underset{R_2 \text{ high}}{\overset{R_1 \text{ both}}{=}} 3.31 V$$

$$\begin{aligned} V_{out} \underset{R_2 \text{ high}}{\overset{R_1 \text{ low}}{=}} & \boxed{3.42 V} \\ V_{out} \underset{R_2 \text{ low}}{\overset{R_1 \text{ high}}{=}} & \boxed{3.19 V} \end{aligned}$$

$$V_{out} \frac{R_1 \text{ low}}{R_2 \text{ high}} = I_{tot} R_{pot} \Rightarrow I_{tot} = \frac{R_2}{R_1 + R_2} V_{in}$$

#5

2.5V @ 0°C

$$\alpha = \frac{10mV}{^{\circ}C} \times \frac{V}{1000mV} = \frac{0.01mV}{^{\circ}C}$$

$$\Delta T = T_s - T_i = 40 - 0 = 40^{\circ}\text{C}$$

$$\underline{0.01mV} \times 40^{\circ}\text{C} = 0.4V$$

$$V = V_i + \Delta V = 2.5 + 0.4 = 2.9V$$

$$V_{in} = 2.9V$$

$$V_{out} = V_{in} - V_{R1} = 2.9 - V_{R1}$$

$$V_{R1} = I_{tot} \cdot R_1$$

$$I_{tot} = V_{in} / R_{tot}$$

$$R_1 = 209\Omega \quad R_2 = 451.5$$

$$R_{tot} = 660.5\Omega$$

$$I_{tot} = 2.9V / 660.5\Omega$$

$$= 0.0044A$$

$$V_{R1} = 0.0044A (209\Omega)$$

$$= 0.92V$$

$$V_{out} = 2.9 - 0.92V$$

$$= 1.98V$$

$$R_1 = 231\Omega \quad R_2 = 408.5\Omega$$

$$R_{tot} = 639.5\Omega$$

$$I_{tot} = 2.9V / 639.5\Omega$$

$$= 0.0045A$$

$$V_{R1} = 0.0045A (231\Omega)$$

$$= 1.05V$$

$$V_{out} = 2.9 - 1.05V$$

$$= 1.85V$$

Voltage Range

$$= 1.85V - 1.98V$$

#6 Uncert. 1% per °C

$$10\text{mV} = 0.01\text{V}$$

$$1\% : 0.01 \times 0.01 = 0.0001\text{V}$$

$$\Delta T = 40\text{ °C} \text{ so } 40(0.0001) = 0.004\text{V}$$

$$V_{out} = V_{in} - V_{R_1} = 2.5 + V_{calc} - V_{R_1}$$

$$V_{R_1} = I_{tot} R_1$$

$$I_{tot} = V_{in} / R_{tot}$$

$$V_{out} = 2.5\text{V} + V_{calc} - (2.5 + V_{calc}) \frac{R_1}{R_{tot}}$$

• Uncertainty R_{tot}

$$R_{tot} = R_1 + R_2$$

$$\delta_{R_{tot}, R_1} = \delta_{R_1} = 0.05(220\Omega) = 11\Omega$$

$$\delta_{R_{tot}, R_2} = \delta_{R_2} = 0.05(430\Omega) = 21.5\Omega$$

$$\delta_{R_{tot}} = \sqrt{(\delta_{R_{tot}, R_1})^2 + (\delta_{R_{tot}, R_2})^2} = \sqrt{11^2 + 21.5^2}\Omega = \pm 24.15\Omega$$

$$\delta_{V_{out, R_{tot}}} = \frac{(2.5 + V_{calc}) R_1}{(R_{tot})^2} \delta_{R_{tot}} = 0.036\text{V}$$

$$\delta_{V_{out, R_1}} = \frac{-(2.5 + V_{calc})}{R_{tot}} \delta_{R_1} = -0.049\text{V}$$

$$\delta_{V_{out, V_{calc}}} = \delta_{V_{calc}} + \frac{R_1}{R_{tot}} \delta_{V_{calc}} = 0.005\text{V}$$

$$\delta_{V_{out}} = \sqrt{\delta_{V_{out, R_{tot}}}^2 + \delta_{V_{out, R_1}}^2 + \delta_{V_{out, V_{calc}}}^2} = \boxed{\pm 0.06\text{V}}$$