

hw Hint: Output 1 = 31


Example: Design a finite state machine for a keypad lock of an office door.

The door unlocks if the input is:

First : 3 pressed
Then: 1 pressed } \Rightarrow Door unlocks.

The output is Unlock.

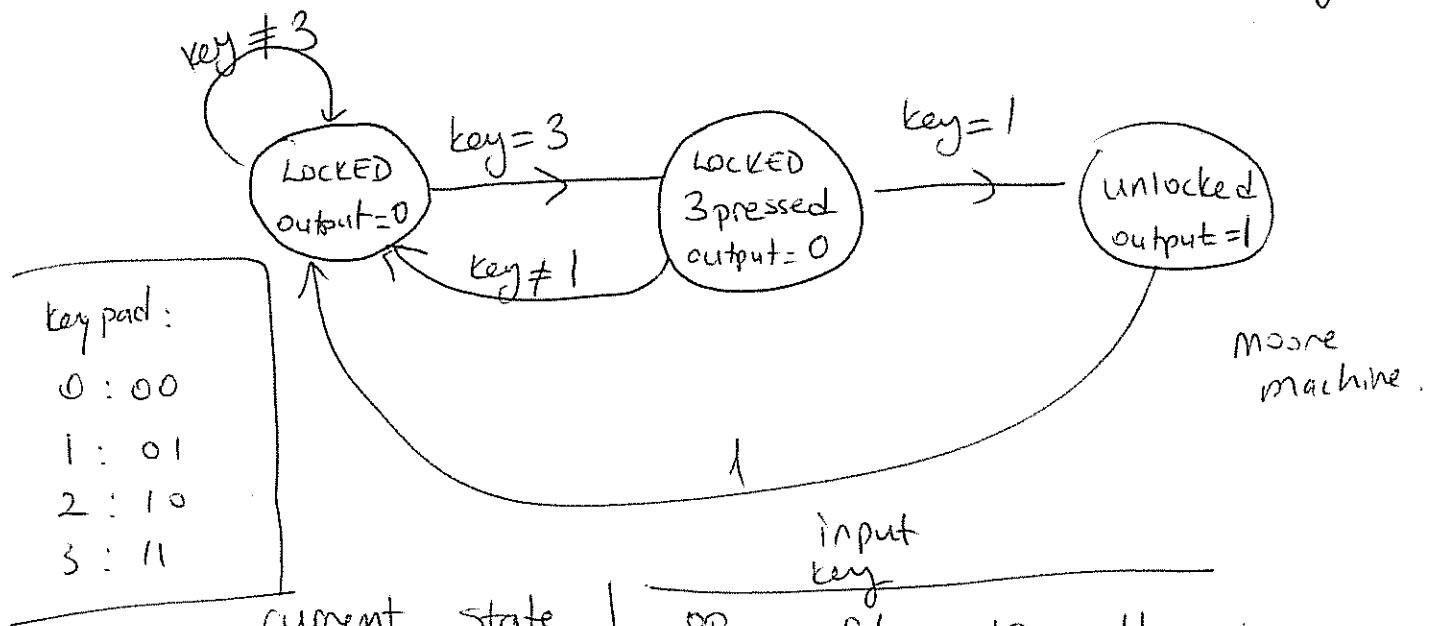Once the door unlocks, it locks back again.



key pad:
0 : 00
1 : 01
2 : 10
3 : 11

| current state | input key | | | |
|------------------|-----------|----------|--------|------------------|
| | 00 | 01 | 10 | 11 |
| LOCKED | LOCKED | LOCKED | LOCKED | LOCKED 3 PRESSED |
| LOCKED 3 PRESSED | LOCKED | UNLOCKED | LOCKED | LOCKED |
| UNLOCKED | LOCKED | LOCKED | LOCKED | LOCKED |

| State Name | Assignment | | | |
|---------------|-------------------|---------------------|------------------|-------------------------|
| | Simplest Q1-Q3 | Decomposed Q1-Q3 | One-Hot Q1-Q5 | Almost One-Hot Q1-Q4 |
| INIT | 000 | 000 | 00001 | 0000 |
| A0 | 001 | 100 | 00010 | 0001 |
| A1 | 010 | 101 | 00100 | 0010 |
| OK0 | 011 | 110 | 01000 | 0100 |
| OK1 | 100 | 111 | 10000 | 1000 |

Table 7-6

Possible state assignments for the state machine in Table 7-5.

state assignments:

Assign binary combination to each named state.

Total number of states in a machine with n flip-flops is 2^n

in our example we have 3 states

$$\log_2 3 \approx 2 \text{ flip-flops}$$

$$\Rightarrow 2^2 = 4 \text{ states}$$

need 3 states

1 state unused.

Simplest state assignment: use first

3 binary integers in binary counting order.

Simplest assignment does not always lead to the simplest excitation equations, output equations and resulting logic circuit.

Practical guidelines for reasonable state assignments:

- Choose initial word state which machine can easily be forced at reset

$(0 \dots 0, 1 \dots 1)$

- Minimize number of state variables that change on each transition.

- Take into account symmetries. If one state means almost the same thing as another \Rightarrow similar assignments differing only one bit.

- If there are unused states \Rightarrow don't limit choice to first s n -bit integers.

- use more than minimum # of state variables

(example): 3 states \Rightarrow use binary counting order for state assignments!

LOCKED = 00 LOCKED/3 = 01

UNLOCKED = 10

| current state q1 q0 | input (A1 A0) | | | | output | |
|------------------------|-------------------|----|----|----|--------|---|
| | 00 | 01 | 10 | 11 | | |
| 00 | 00 | 00 | 00 | 01 | 0 | |
| 01 | 00 | 10 | 00 | 00 | 0 | |
| 10 | 00 | 00 | 00 | 00 | 1 | |
| q1* q0* | | | | | | |
| unused state | 11 (minimal risk) | 00 | 00 | 00 | 00 | 0 |
| | 11 (minimal cost) | xx | xx | xx | xx | 0 |

unused states:

1) minimal risk: for any input condition the unused state goes to initial/ idle/ safe state.

2) minimal cost: assume no entry to the unused states \Rightarrow mark them as don't cares.

Form k-maps to find the transition eqn.

$Q1^*$:

| | | | | | |
|--------|--------|----|----|----|----------------------|
| $A1A0$ | | | | | |
| $Q1Q0$ | | 00 | 01 | 11 | 10 |
| 00 | | | | | |
| 01 | | | 1 | | |
| 11 | used → | X | X | X | X ← for minimal cost |
| 10 | | | | | |

For minimal risk:

$$Q1^* = Q1' Q0 A1' A0$$

For minimal cost:

$$Q1^* = A1' A0 Q0$$

transition equations

$$Q0^* = Q1' Q0' A1 A0$$

Excitation eqns:

$$D1 = Q1^* , D0 = Q0^*$$

Output eqn: $UNLOCKED = Q1 \cdot Q0'$

