

EECS 281, January 27, 2015

Noninverting Gates:

In CMOS: simplest gates are inverters
and next simplest are NAND
and NOR gates.

Not possible to design a noninverting
gate with a smaller number of
transistors than an inverting one.

Switching Algebra

X : variable, represents conditions of
a logic signal.

low/high, on/off, 0/1

Axioms:

$A1: X=0 \text{ if } X \neq 1$

$A1': X=1 \text{ if } X \neq 0$

$$A2: \text{ If } X=0, \text{ then } X'=1$$

$$A2': \text{ If } X=1, \text{ then } X'=0$$

(In a logic expression: multiplication has precedence)

$$\text{e.g. } w \cdot x + y \cdot z = (w \cdot x) + (y \cdot z)$$

$$A3: 0 \cdot 0 = 0$$

$$A3': 1 + 1 = 1$$

$$A4: 1 \cdot 1 = 1$$

$$A4': 0 + 0 = 0$$

$$A5: 0 \cdot 1 = 1 \cdot 0 = 0$$

$$A5': 1 + 0 = 0 + 1 = 1$$

$A1 - A5$ and $A1' \text{ to } A5'$ completely define switching algebra

single-Variable Theorems

$$T1: X + 0 = X$$

Proof by perfect induction:

$$X=0 \quad \overset{X}{0} + 0 = \overset{X}{0} \text{ true by } A4'$$

$$T1': X \cdot 1 = X$$

$$\left. \begin{array}{l} T2: X + 1 = 1 \\ T2': X \cdot 0 = 0 \end{array} \right\} \text{ (Null elements)}$$

$$\text{(Idempotency)} T3: X + X = X \quad T3': X \cdot X = X$$

$$T4: (X')' = X \quad \text{(Involution)}$$

$$\text{(Complements)} T5: X + X' = 1 \quad T5': X \cdot X' = 0$$

$$T6: X + Y = Y + X \quad T6': X \cdot Y = Y \cdot X$$

Commutativity.

$$\begin{array}{l} T7: (X + Y) + Z = X + (Y + Z) \\ T7': (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z) \end{array} \quad \text{Associativity}$$

~~Distributivity~~ Distributivity:

$$T8: X \cdot Y + X \cdot Z = X \cdot (Y + Z)$$

$$T8': (X + Y) \cdot (X + Z) = X + Y \cdot Z$$

Covering:

$$X \cdot (\underbrace{1 + 1}_{1}) = X$$

$$T_9: X + X \cdot Y = X$$

Combining:

$$X \cdot (\overbrace{Y + Y'}^1) = X$$

$$T_{10}: X \cdot Y + X \cdot Y' = X$$

$$T_{10}': (X + Y) \cdot (X + Y') = X$$

Can sensus:

$$T_{11}: X \cdot Y + X' \cdot Z + Y \cdot Z = \\ X \cdot Y + X' \cdot Z$$

$$Y \cdot Z = 0 \quad \frac{X \cdot Y + X' \cdot Z + 0}{X \cdot Y + X' \cdot Z} =$$

$$Y \cdot Z = 1 \Rightarrow \underbrace{Y = 1, Z = 1}$$

$$\begin{aligned} X &= 0 \\ Y &= 1 \\ Z &= 1 \end{aligned}$$

$$X \cdot Y + X' \cdot Z = 1$$

$$x=1$$

$$x \cdot y + x' \cdot z = 1$$

$$y=1$$

$$z=1$$


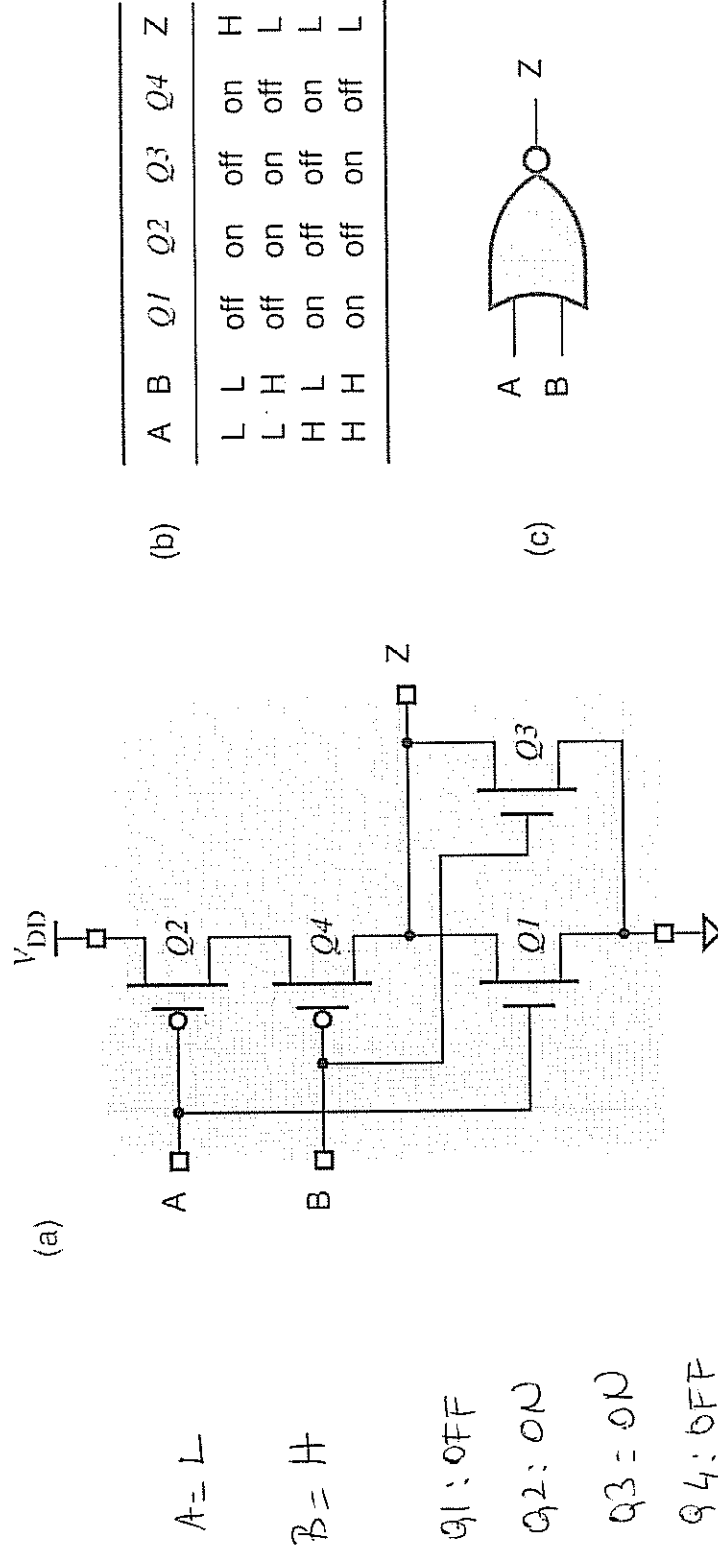


Figure 3-15

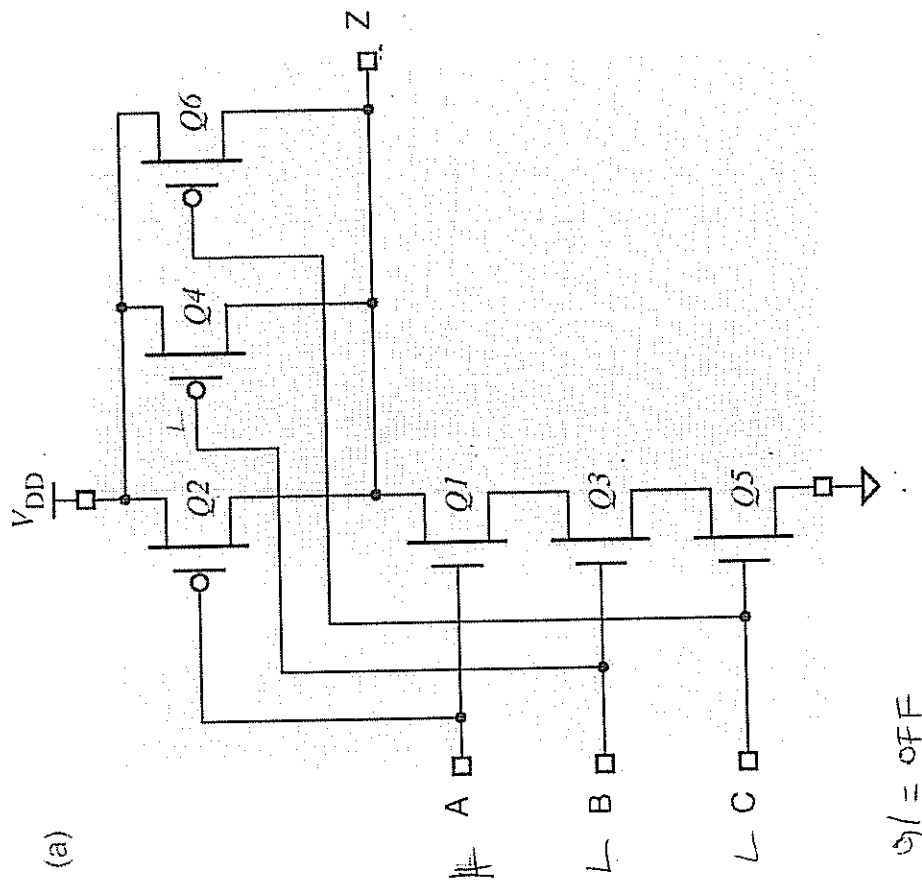CMOS 2-input NOR gate: (a) circuit diagram; (b) function table; (c) logic symbol.



(b)

A	B	C	Q1	Q2	Q3	Q4	Q5	Q6	Z
L	L	L	off	on	off	on	off	on	H
L	L	H	off	on	off	on	on	off	H
L	H	L	off	on	on	off	off	on	H
L	H	H	off	on	on	off	on	off	H
H	L	L	on	off	off	on	off	on	H
H	L	H	on	off	off	on	on	off	H
H	H	L	on	off	on	off	off	on	H
H	H	H	on	off	on	off	on	off	L

(c)


 


Figure 3-16

 CMOS 3-input NAND gate: (a) circuit diagram; (b) function table; (c) logic symbol.



(b)

A	Q1	Q2	Q3	Q4	Z
L	off	on	on	off	L
H	on	off	off	on	H



Figure 3-18

CMOS noninverting buffer: (a) circuit diagram; (b) function table; (c) logic symbol.

$A = L$
 $Y = H$
 $Z = L$


 


Figure 3-19

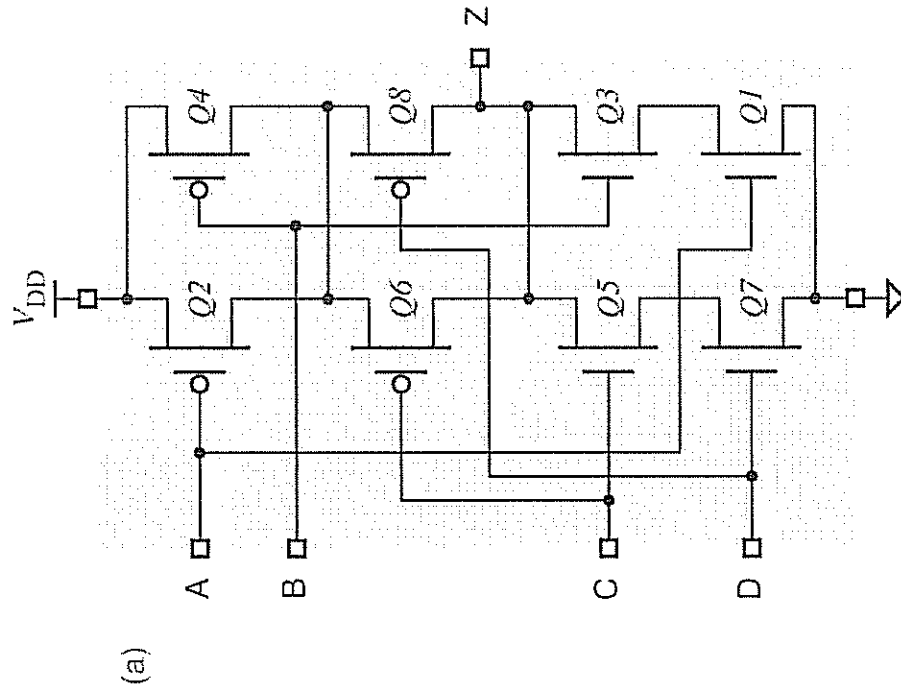CMOS 2-input AND gate: (a) circuit diagram; (b) function table; (c) logic symbol.



(b)

A	B	C	D	Q1	Q2	Q3	Q4	Q5	Q6	Q7	Q8	Z
L	L	L	L	off	o	off	on	off	on	off	on	H
L	L	L	H	off	o	off	on	off	on	o	off	H
L	L	H	L	off	o	off	on	o	off	off	on	H
L	L	H	H	off	o	off	on	o	off	o	off	L
L	H	L	L	off	o	o	off	off	on	off	on	H
L	H	L	H	off	o	o	off	off	on	o	off	H
L	H	H	L	off	o	o	off	o	off	off	on	H
L	H	H	H	off	o	o	off	o	off	o	off	L
H	L	L	L	o	off	off	on	off	on	off	on	H
H	L	L	H	o	off	off	on	off	on	on	off	H
H	L	H	L	o	off	off	on	o	off	off	on	H
H	L	H	H	o	off	off	on	o	off	on	off	L
H	H	L	L	o	off	o	off	o	off	off	on	L
H	H	L	H	o	off	o	off	off	on	on	off	L
H	H	H	L	o	off	o	off	o	off	off	on	L
H	H	H	H	o	off	o	off	o	off	off	off	L

Figure 3-20
CMOS AND-OR-INVERT gate: (a) circuit diagram; (b) function table.

For simplicity assume: $t_r = t_f = 0$.

t_p can be different depending on direction of change.

4.5

 


Figure 3-42

Propagation delays for a CMOS inverter: (a) ignoring rise and fall times; (b) measured at midpoints of transitions.