

XVIII. Logic and Bit Operations in Hardware

- A. Each of the logical operations discussed previously (among others) can be implemented in computer hardware.
- B. Since binary computers implement bit manipulations, the truth value *true* corresponds to the value $1B$ (the bit is turned on) and the truth value false corresponds to the value $0B$ (the bit is turned off).
- C. Hardware Representation of Truth Values:
 1. *true* corresponds to a switch that is turned on while *false* corresponds to a switch that is turned off.
 2. *true* corresponds to a voltage of $+5$ volts while *false* corresponds to a voltage of -5 volts.
 3. *true* corresponds to a binary 1, or one bit turned on, while *false* corresponds to a binary 0, or one bit turned off.

D. Bit Operations

		Disjunction	Conjunction	Exclusive Or
x	y	$x \vee y$	$x \wedge y$	$x \oplus y$
1	1	1	1	0
1	0	1	0	1
0	1	1	0	1
0	0	0	0	0

E. Bit String Operations:

1. Normally these operations accept strings of bits as operands rather than single bits.

$$2. \quad \text{Example: } 219_{10} = 110011011_2$$

$$= 1 \times 2^7 + 1 \times 2^6 + 1 \times 2^4 \\ + 1 \times 2^3 + 1 \times 2^1 + 1 \times 2^0$$

$$= 64 + 16 + 8 + 2 + 1 = 219$$


$$125_{10} = 001111101_2$$

3. Then: $219 \vee 125 = 110011011_2 \vee 001111101_2$
 $= 11111111_2 = 255_{10}$


4. And: $219 \wedge 125 = 110011011_2 \wedge 001111101_2$
 $= 000011001_2 = 25_{10}$

XIX. BitWise Compound Propositions Implemented in Hardware

 A. The hardware symbol for the conjunction of P and Q is:



 
B. The hardware symbol for the disjunction of P and Q is:




C. In both of the above the binary input for P , either '1'B (true) or '0'B (false), enters via the upper arrow (an electrical connection) while the the binary input for Q , either '1'B (true) or '0'B (false), enters via the upper arrow.

D. The output for either $P \wedge Q$ or $P \vee Q$, either '1'B (true) or '0'B (false) emerges from the right-most arrow.

 H. The hardware symbol for the negation of P , or $\neg P$, is:



 so $\neg(P \vee Q)$ would be represented in hardware as:




XIX. Representing Compound Logical Expressions in Hardware

A. Consider the logical expression:

$$(P \wedge \neg Q) \vee (R \wedge \neg Q) \vee \neg(P \wedge \neg R)$$

 
B. This expression can be represented in hardware as shown below:



- C. The left-most column of hardware gates represents, from top-to-bottom:
1. $P \wedge \neg Q$
 2. $R \wedge \neg Q$
 3. $P \wedge \neg R$
- D. The center column of hardware gates represents, from top-to-bottom:
1. $(P \wedge \neg Q) \vee (R \wedge \neg Q)$
 2. $\neg(P \wedge \neg R)$
- E. The right-most column, a single gate, represents:
 $((P \wedge \neg Q) \vee (R \wedge \neg Q)) \vee \neg(P \wedge \neg R)$

XX. Binary Addition Implemented in Hardware

A. Circuit

 

B. Bit Addition Definition

A	B	Sum	$Carry$
1	1	0	1
1	0	1	0
0	1	1	0
0	0	0	0