 


EECS 281, March 26, 2015

Example: state machine that controls tail lights of a car.



For turns Two input signals: LEFT, RIGHT.

Emergency flasher: input HAZ or LEFT or RIGHT at the same time
all tail lights are on.

Free running clock signal with freq. of desired flashing rate.


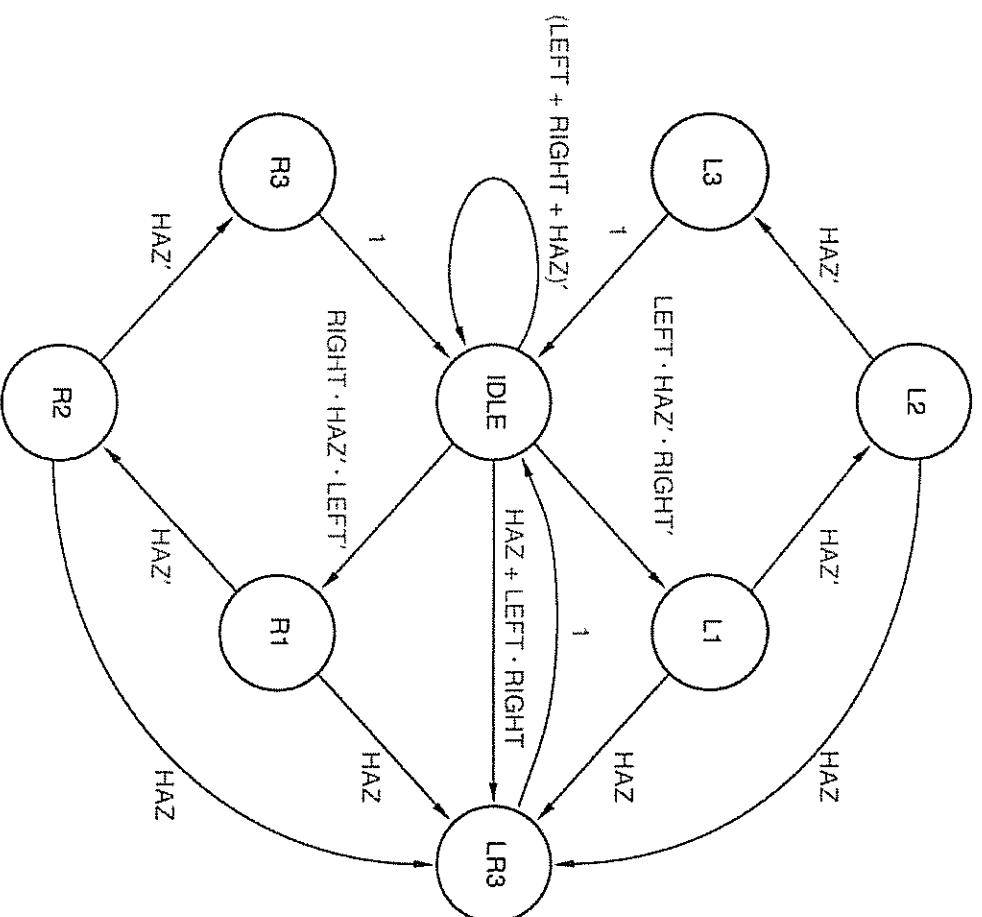


Figure 7-58

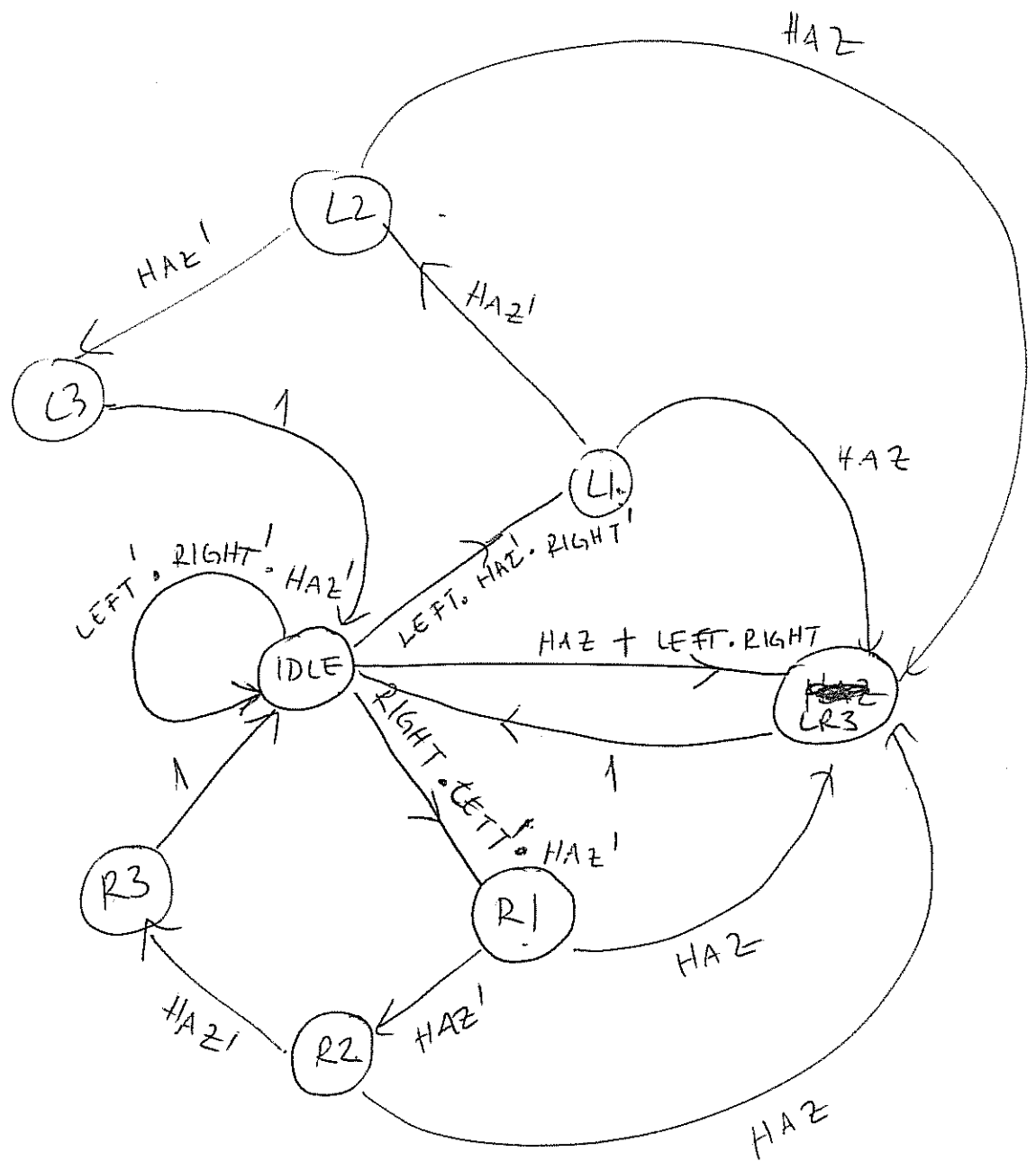Enhanced state diagram for T-bird tail lights.



output table

state	outputs						
	LC	LB	LA	RA	RB	RC	
IDLE	0	0	0	0	0	0	
L1	0	0	1	0	0	0	
L2	0	1	1	0	0	0	
L3	1	1	1	0	0	0	
⋮							
LR3	1	1	1	1	1	1	

$$LA = L + L2 + L3 + LR3$$

$$LB = L2 + L3 + LR3$$

$$LC = L3 + LR3$$

⋮

I have 8 states \Rightarrow will need a minimum of 3 flip-flops.

state assignment:

state	q2	q1	q0
IDLE	0	0	0
L1	0	0	1
L2	0	1	1
L3	0	1	0
R1	1	0	1
R2	1	1	1
R3	1	1	0
LR3	1	0	0

$$Q1X = Q2' \cdot Q1' \cdot Q0 \cdot HAZ' + Q2' \cdot Q1 \cdot Q0 \cdot HAZ' + Q2 \cdot Q1' \cdot Q0 \cdot HAZ' + Q2 \cdot Q1 \cdot Q0 \cdot HAZ'$$

S	Q2	Q1	Q0	Transition Expression	S	Q2	Q1	Q0
IDLE	0	0	0	(LEFT + RIGHT + HAZ)'	IDLE	0	0	0
IDLE	0	0	0	LEFT · HAZ' · RIGHT'	L1	0	0	1
IDLE	0	0	0	HAZ + LEFT · RIGHT	LR3	1	0	0
IDLE	0	0	0	RIGHT · HAZ' · LEFT'	R1	1	0	1
L1	0	0	1	HAZ'	L2	0	1	1
L1	0	0	1	HAZ	LR3	1	0	0
L2	0	1	1	HAZ'	L3	0	1	0
L2	0	1	1	HAZ	LR3	1	0	0
L3	0	1	0	1	IDLE	0	0	0
R1	1	0	1	HAZ'	R2	1	1	1
R1	1	0	1	HAZ	LR3	1	0	0
R2	1	1	1	HAZ'	R3	1	1	0
R2	1	1	1	HAZ	LR3	1	0	0
R3	1	1	0	1	IDLE	0	0	0
LR3	1	0	0	1	IDLE	0	0	0

Table 7-14

Transition list for T-bird tail-lights state machine.

$$LA = 1 \quad \text{when} \quad L1 + L2 + L3 + LR3$$

Output table LA

	$Q2$	$Q1$	$Q0$	LA
$L1 \rightarrow$	0	0	1	1
$L2 \rightarrow$	0	1	1	1
$L3 \rightarrow$	0	1	0	1
$LR3 \rightarrow$	1	0	0	1

K-map:

$Q2 \backslash Q1 \backslash Q0$	00	01	11	10
0	0	1	0	1
1	1	1	0	0

$$LA = Q2' \cdot Q0 + Q2' \cdot Q1 + Q2 Q1' \cdot Q0'$$


Register: a collection of two or more
D flip-flops with a common clock
input.

often used to store a collection
of related bits.

Counters:

Any clocked sequential circuit
with state diagram containing a single
cycle.

e.g.

 

modulo-m
counter /
divide-by-
m counter.

Modulus of a counter: # of states
in the cycle.

 
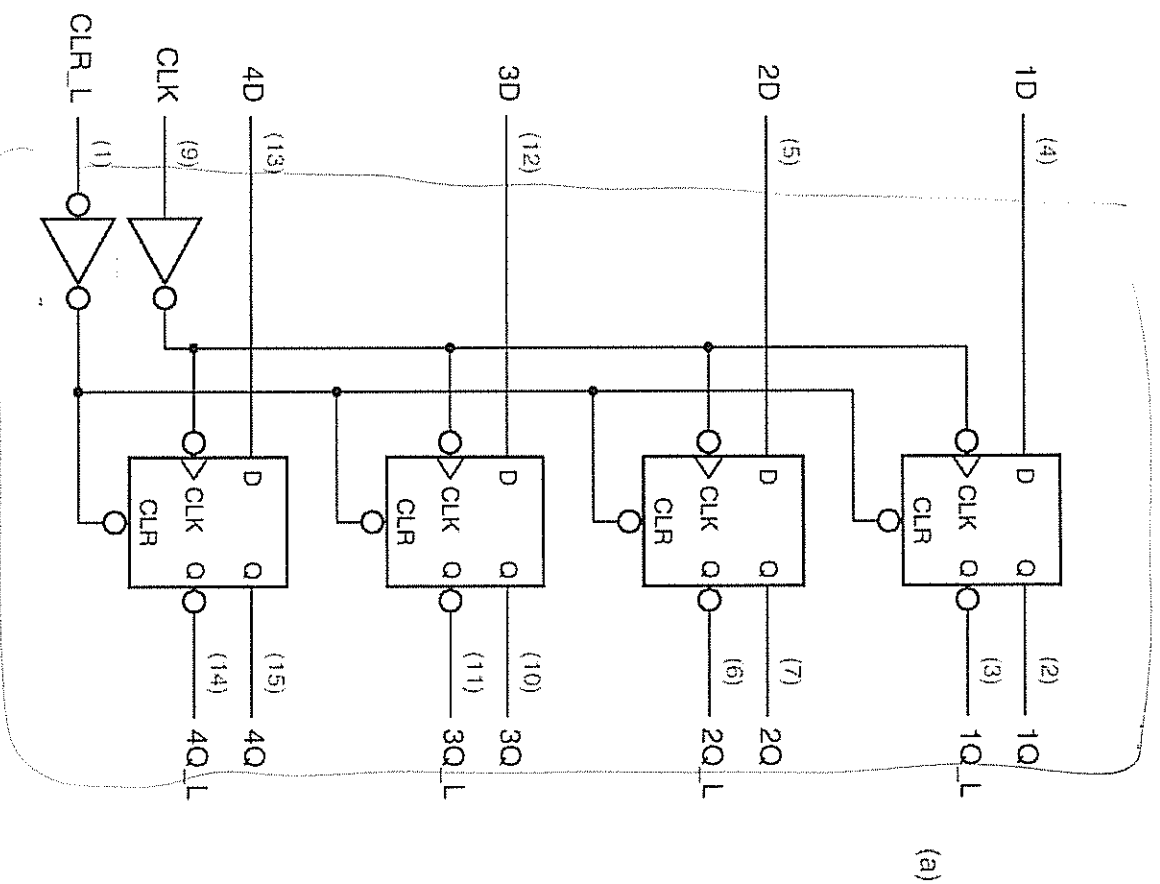


Figure 8-8

The 74x175 4-bit register: (a) Logic diagram, including pin numbers for a standard 16-pin dual in-line package; (b) traditional logic symbol.


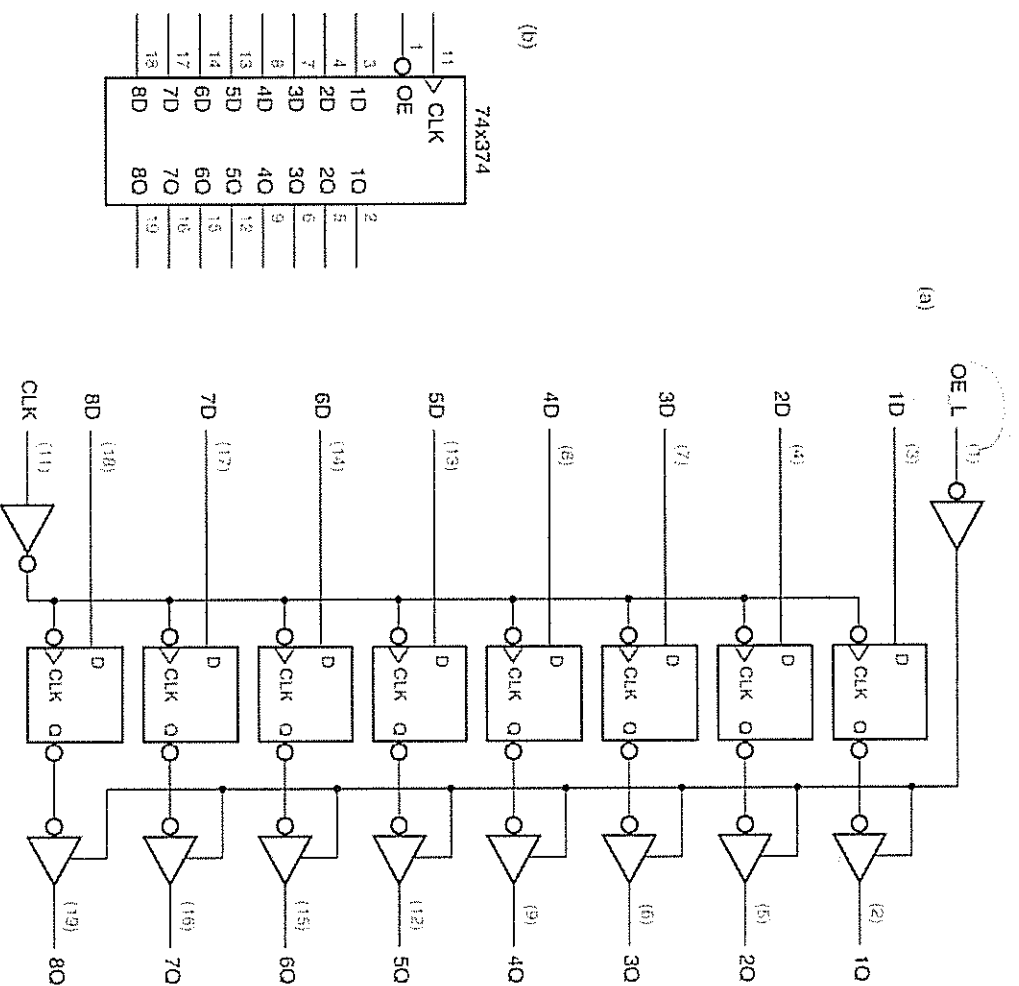



Figure 8-10

The 74x374 8-bit register: (a) logic diagram, including pin numbers for a standard 20-pin dual in-line package;
 (b) traditional logic symbol.

Ripple counters :

 

T flip-flop changes state (toggles) on every rising edge of its clock input.

 

 


Figure 8-25

A synchronous 4-bit binary counter with serial enable logic.