

EECS 281 January 22, 2015

Subtraction:

two's complement numbers:

negate subtrahend by taking
two's complement, then add it to
the minuend.

$$\begin{array}{r} 4 \\ - 3 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 0100 \\ - 0011 \\ \hline \end{array}$$

$$\begin{array}{r} 0100 \\ + 1101 \\ \hline 10001 \end{array}$$


$$\begin{array}{r} 0011 \leftarrow 3 \\ + 1100 \\ \hline 1101 \leftarrow -3 \end{array}$$

$$\begin{array}{r} 0100 \text{ (1) } \leftarrow \text{in} \\ + 1100 \\ \hline \end{array}$$

overflow: examine the signs of minuend and
complemented of subtrahend: same
rules apply as in addition.

Digital Circuits:

 Map real values for physical quantities into two logic values 0 and 1.




Combinational circuit: outputs depend only on its current inputs.

operation fully defined by a truth table.


Sequential circuit: circuit with memory, outputs depend on current input and sequence of past inputs.

 Three basic logic functions: AND, OR, NOT
 can be used to build any combinational
 digital logic circuit.




$$\frac{2}{2} = 4$$

X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1

 


X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1

 


X	NOT X
0	1
1	0

NAND: NOT - AND

 

X	Y	$X \text{ NAND } Y$
0	0	1
0	1	1
1	0	1
1	1	0

 

X	Y	$X \text{ NOR } Y$
0	0	1
0	1	0
1	0	0
1	1	0

 


Figure 3-4

Logic circuit with the truth table of Table 3-2.

$$F = X \cdot Y + X' \cdot Y' \cdot Z$$

$$X=0, Y=0, Z=0 \quad F = 0 \cdot 0 + 1 \cdot 1 \cdot 0 = 0$$

logic signals : do not change from 0 \rightarrow 1 instantaneously
lag between input change and corresponding output change.

 




Figure 3-5

Timing diagram for a logic circuit.




CMOS logic circuits

building blocks MOS transistors.

  modeled them as 3-terminal device that acts like a voltage controlled resistance.





e.g. $V_{in} = 0$

   

MOS transistors \rightarrow n-channel
 \searrow p-channel

n-channel : NMOS

  

normally $V_{gs} \geq 0$

increase $V_{gs} \Rightarrow$ decrease R_{ds}

$V_{gs} = 0 \Rightarrow R_{ds} = \text{very high.}$


$V_{in} = H = 5V \Rightarrow$ switch is closed.

p-channel : PMOS







$V_{in} = L$

switch is closed.

 

   $\frac{1}{7} \downarrow :$
 ground = 0'
 = L



 

A	B	Q1	Q2	Q3	Q4	Z
L	L	OFF	ON	OFF	ON	H
L	H	OFF	ON	ON	OFF	H
H	L	ON	OFF	OFF	ON	H
H	H	ON	OFF	ON	OFF	L